
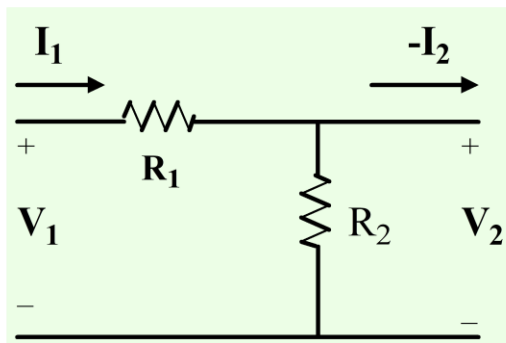


Q1.

Consider the following network:

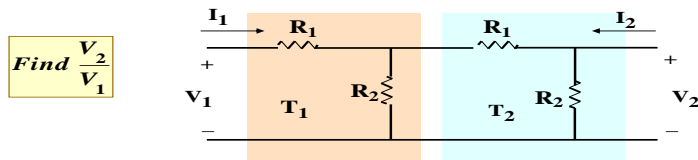

We can write the following equations.

$$V_1 = (R_1 + R_2)I_1 + R_2I_2$$

$$V_2 = R_2I_1 + R_2I_2$$

It is not always possible to write 2 equations in terms of the V's and I's  
Of the parameter set.

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{bmatrix} \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

## Interconnection Of Two Port Networks

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{bmatrix} \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$


Multiply out the first row:

$$V_1 = \left[ \left[ \left( \frac{R_1 + R_2}{R_2} \right)^2 + \frac{R_1}{R_2} \right] V_2 + \left[ \left( \frac{R_1 + R_2}{R_2} \right) R_1 + R_1 \right] (-I_2) \right]$$


Set  $I_2 = 0$  ( as in the diagram)

$$\frac{V_2}{V_1} = \frac{R_2^2}{R_1^2 + 3R_1 R_2 + R_2^2}$$

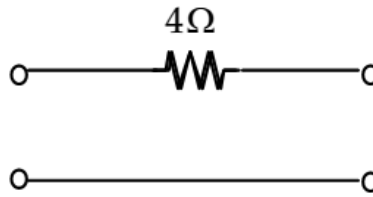Can be verified directly  
by solving the circuit



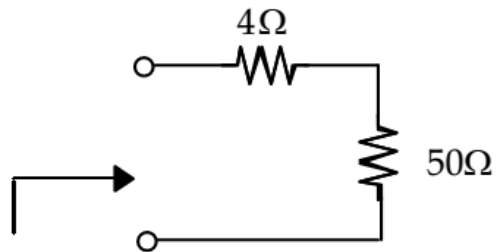Given  $Z_0 = 50\Omega$ , what is  $S_{11}$ ?




$$Z_{in}|_{Z_L=Z_0} = 54\Omega$$

$$S_{11} = \frac{54 - 50}{54 + 50} = \frac{4}{104}$$


Similar arguments give  $S_{22} = \frac{4}{104}$ .

**Find  $S_{21}$**

$$S_{21} = \frac{b_2}{a_1} |_{a_2=0}$$

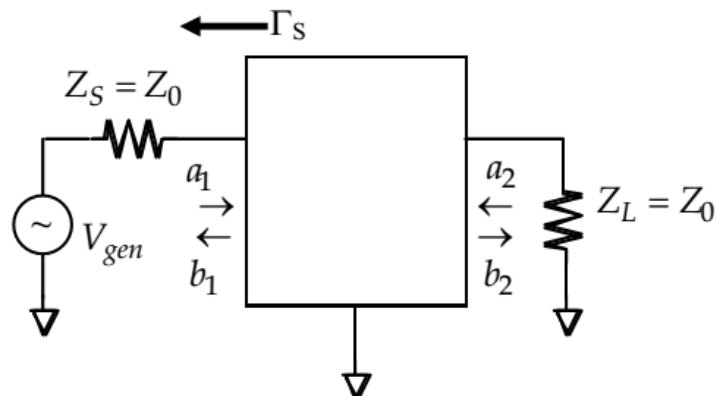

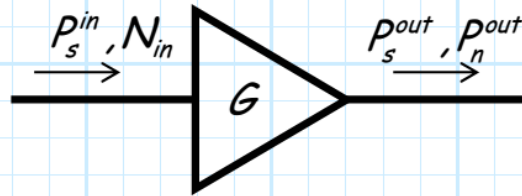Say the **power** of this input signal is  $P_s^{in}$ . The output of the amplifier will therefore include **both** a signal with power  $P_s^{out}$ , and noise with power  $P_n^{out}$ :



where:

$$P_s^{out} = G P_s^{in}$$

and:

$$\begin{aligned} P_n^{out} &= N_{in} + G k T_e B \\ &= G k (T_{in} + T_e) B \end{aligned}$$

In order to accurately demodulate the signal, it is important that signal power be **large** in comparison to the noise power.

Thus, a fundamental and important measure in radio systems is the **Signal-to-Noise Ratio (SNR)**:

$$SNR \doteq \frac{P_s}{P_n}$$

The larger the SNR, the better!

At the **output** of the amplifier, the SNR is:

$$\begin{aligned} SNR_{out} &= \frac{P_s^{out}}{P_n^{out}} \\ &= \frac{G P_s^{in}}{G k (T_{in} + T_e) B} \\ &= \frac{P_s^{in}}{k (T_{in} + T_e) B} \end{aligned}$$

Moreover, we can define an **input noise power** as the total noise power across the **bandwidth of the amplifier**:

$$P_n^{in} = N_{in} B = k T_{in} B$$

And thus the **input SNR** as:

$$SNR_{in} = \frac{P_s^{in}}{P_n^{in}} = \frac{P_s^{in}}{k T_{in} B}$$

Now, let's take the **ratio** of the input SNR to the output SNR:

$$\begin{aligned} \frac{SNR_{in}}{SNR_{out}} &= \frac{P_s^{in}}{k T_{in} B} \left( \frac{k (T_{in} + T_e) B}{P_s^{in}} \right) \\ &= \frac{T_{in} + T_e}{T_{in}} \\ &= 1 + \frac{T_e}{T_{in}} \end{aligned}$$

Thus, the **Noise Figure** ( $F$ ) of a device is defined as:


$$\begin{aligned} F &\doteq \frac{SNR_{in}}{SNR_{out}} \bigg|_{T_{in}=290K^{\circ}} \\ &= \left( 1 + \frac{T_e}{T_{in}} \right) \bigg|_{T_{in}=290K^{\circ}} \\ &= 1 + \frac{T_e}{290K^{\circ}} \end{aligned}$$

3a)

$P_{AVS} = \text{max power output from a source with impedance } Z_S \text{ that can be absorbed into a load.}$


let  $Z_S = Z_0$ ,  $Z_L = Z_S^* = Z_0$  (in this case)

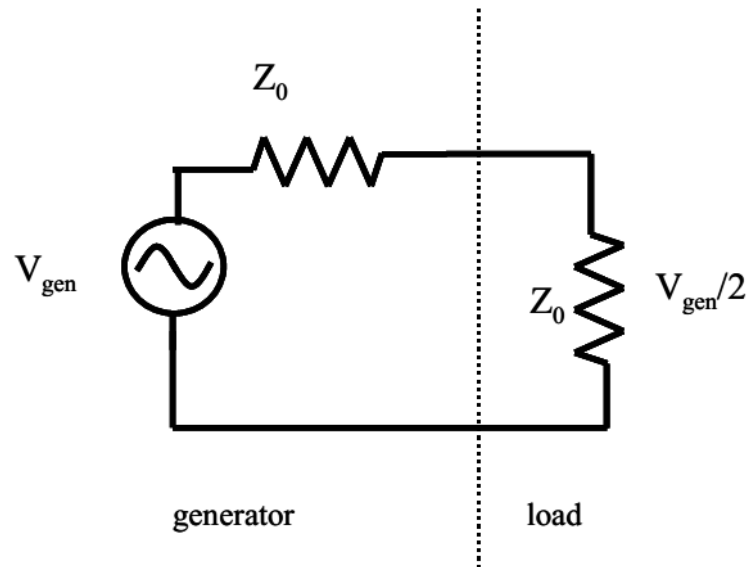because maximum power transfer occurs when we have a conjugate match



$$P_{load} = P_{AVS} = \frac{1}{8} \frac{V_{gen}^2}{Z_0}$$

Or, in terms of a and b:

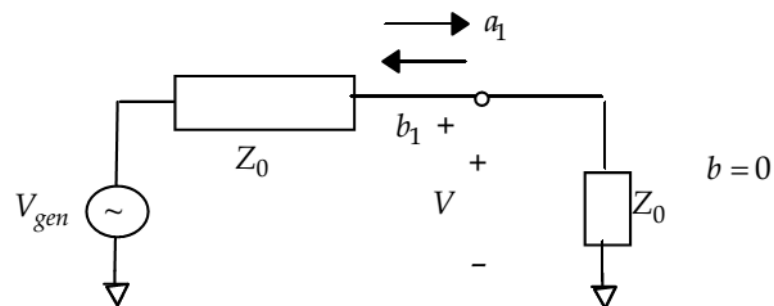

$$a_1 = \frac{V^+}{\sqrt{Z_0}} \text{ and } b_1 = 0; \quad V^+ = V_{gen} \left( \frac{Z_0}{Z_0 + Z_0} \right) = \frac{V_{gen}}{2} \text{ and } V^- = 0$$

So,

$$P_{load} = P_{AVS} = \frac{1}{2} a_1 a_1^* = \frac{V_{gen}^2}{8Z_0}$$

### Actual Load Power

$$P_{\text{Load}} = \frac{1}{2}|a_1|^2 - \frac{1}{2}|b_1|^2 = \frac{1}{2}\text{Re}[I_1 V_1^*]$$

or

$$P_{\text{Load}} = P_{\text{AVS}}(1 - |S_{11}|^2)$$

### Reflected Power

$$b_1 = a_1 S_{11}$$

$$P_R = \frac{1}{2}|b_1|^2 = \frac{1}{2}|a_1|^2 |S_{11}|^2 = P_{\text{AVS}} |S_{11}|^2$$

$$|S_{11}|^2 = \frac{\text{Power reflected from input}}{\text{Power incident on input}} = \frac{|b_1|^2}{|a_1|^2}$$

$$|S_{22}|^2 = \frac{\text{Power reflected from network output}}{\text{Power incident on output}} = \frac{|b_2|^2}{|a_2|^2}$$

Similarly,


$$\begin{aligned} \frac{1}{2}|a_2|^2 &= \text{Power incident on output} \\ &= \text{Reflected power from load} \end{aligned}$$

$$\frac{1}{2}|b_1|^2 = \text{Power reflected from input port}$$

$$\frac{1}{2}|b_2|^2 = \text{Power incident on load from the network}$$



## Terminated Transmission Line

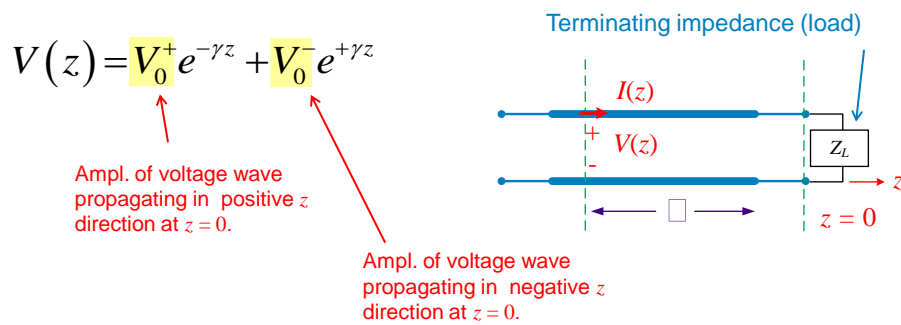

Where do we assign  $z = 0$ ?

The usual choice is at the load.

Note: The length  $l$  measures distance from the load:  $l = -z$

1

## Terminated Transmission Line (cont.)

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

What if we know

$V^+$  and  $V^-$  @  $z = -l$

Can we use  $z = -l$  as a reference plane?

$$V_0^+ = V^+(0) = V^+(-l) e^{-\gamma l}$$

$$V^-(-l) = V^-(0) e^{-\gamma l}$$

$$\Rightarrow V_0^- = V^-(-l) = V^-(-l) e^{\gamma l}$$

Hence

$$V(z) = V^+(-l) e^{-\gamma(z+l)} + V^-(-l) e^{\gamma(z+l)}$$

34


## Terminated Transmission Line (cont.)

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

What if we know

$V^+$  and  $V^-$  @  $z = -l$

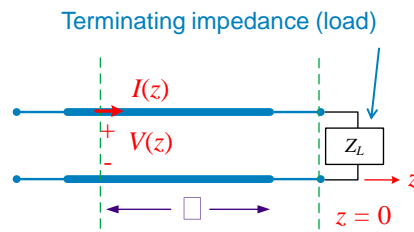Can we use  $z = -l$  as  
a reference plane?



$$V_0^+ = V^+(-l) = V^+(0) e^{-\gamma l}$$

$$V^-(-l) = V^-(0) e^{-\gamma l}$$

$$\Rightarrow V_0^- = V^-(-l) = V^-(0) e^{-\gamma l}$$

Hence

$$V(z) = V^+(-l) e^{-\gamma(z+l)} + V^-(-l) e^{\gamma(z+l)}$$

34

## Terminated Transmission Line (cont.)


$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

What is  $V(-l)$ ?

$$V(-l) = V_0^+ e^{\gamma l} + V_0^- e^{-\gamma l}$$

propagating  
forwards

propagating  
backwards

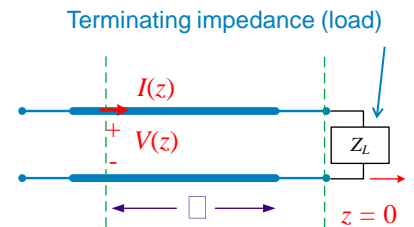


The current at  $z = -l$  is then

$$I(-l) = \frac{V_0^+}{Z_0} e^{\gamma l} - \frac{V_0^-}{Z_0} e^{-\gamma l}$$

$l \equiv$  distance away from load

36

## Terminated Transmission Line (cont.)

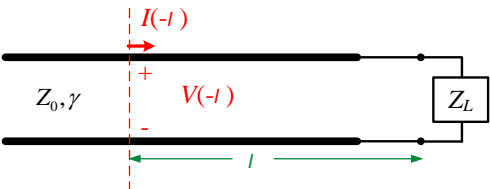

Total volt. at distance  $l$  from the load

$$V(-l) = V_0^+ e^{\gamma l} + V_0^- e^{-\gamma l} = V_0^+ e^{\gamma l} \left( 1 + \frac{V_0^-}{V_0^+} e^{-2\gamma l} \right)$$

Ampl. of volt. wave prop. towards load, at the load position ( $z = 0$ ).      Ampl. of volt. wave prop. away from load, at the load position ( $z = 0$ ).       $\Gamma_L \equiv$  Load reflection coefficient

$\Gamma_l \equiv$  Reflection coefficient at  $z = -l$


$$= V_0^+ e^{\gamma l} (1 + \Gamma_L e^{-2\gamma l})$$

Similarly,

$$I(-l) = \frac{V_0^+}{Z_0} e^{\gamma l} (1 - \Gamma_L e^{-2\gamma l})$$

37

## Terminated Transmission Line (cont.)

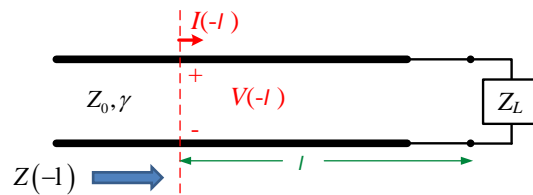

$$V(-l) = V_0^+ e^{\gamma l} (1 + \Gamma_L e^{-2\gamma l})$$

$$I(-l) = \frac{V_0^+}{Z_0} e^{\gamma l} (1 - \Gamma_L e^{-2\gamma l})$$

$$Z(-l) = \frac{V(-l)}{I(-l)} = Z_0 \left( \frac{1 + \Gamma_L e^{-2\gamma l}}{1 - \Gamma_L e^{-2\gamma l}} \right)$$

Input impedance seen "looking" towards load at  $z = -l$ .

38

## Terminated Transmission Line (cont.)

At the load ( $l = 0$ ):

$$Z(0) = Z_0 \left( \frac{1 + \Gamma_L}{1 - \Gamma_L} \right) \equiv Z_L \quad \Rightarrow \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Recall  $Z(-l) = Z_0 \left( \frac{1 + \Gamma_L e^{-2\gamma l}}{1 - \Gamma_L e^{-2\gamma l}} \right)$

Thus,

$$Z(-l) = Z_0 \left( \frac{1 + \left( \frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma l}}{1 - \left( \frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma l}} \right)$$

39

## Terminated Transmission Line (cont.)

Simplifying, we have

$$\begin{aligned} Z(-l) &= Z_0 \left( \frac{1 + \left( \frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma l}}{1 - \left( \frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma l}} \right) = Z_0 \left( \frac{(Z_L + Z_0) + (Z_L - Z_0) e^{-2\gamma l}}{(Z_L + Z_0) - (Z_L - Z_0) e^{-2\gamma l}} \right) \\ &= Z_0 \left( \frac{(Z_L + Z_0) e^{+\gamma l} + (Z_L - Z_0) e^{-\gamma l}}{(Z_L + Z_0) e^{+\gamma l} - (Z_L - Z_0) e^{-\gamma l}} \right) \\ &= Z_0 \left( \frac{Z_L \cosh(\gamma l) + Z_0 \sinh(\gamma l)}{Z_0 \cosh(\gamma l) + Z_L \sinh(\gamma l)} \right) \end{aligned}$$

Hence, we have

$$Z(-l) = Z_0 \left( \frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)} \right)$$

40

## Terminated Lossless Transmission Line

$$\gamma = \cancel{\alpha} + j\beta = j\beta$$

$$V(-l) = V_0^+ e^{j\beta l} (1 + \Gamma_L e^{-2j\beta l})$$

$$I(-l) = \frac{V_0^+}{Z_0} e^{j\beta l} (1 - \Gamma_L e^{-2j\beta l})$$

$$Z(-l) = Z_0 \left( \frac{1 + \Gamma_L e^{-2j\beta l}}{1 - \Gamma_L e^{-2j\beta l}} \right)$$

$$Z(-l) = Z_0 \left( \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right)$$

Impedance is periodic  
with period  $\lambda_g/2$

$\tan$  repeats when

$$\beta l = \pi$$

$$\frac{2\pi}{\lambda_g} l = \pi$$

$$\Rightarrow l = \lambda_g / 2$$

Note:  $\tanh(jl) = \tanh(j\beta l) = j \tan(\beta l)$

41

Ans to 4b)

## Quarter-Wave Transformer


$$Z_{in} = Z_{0T} \left( \frac{Z_L + jZ_{0T} \tan \beta l}{Z_{0T} + jZ_L \tan \beta l} \right)$$

$$\beta l = \beta \frac{\lambda_g}{4} = \frac{2\pi}{\lambda_g} \frac{\lambda_g}{4} = \frac{\pi}{2}$$

$$\Rightarrow Z_{in} = Z_{0T} \left( \frac{jZ_{0T}}{jZ_L} \right)$$

so

$$Z_{in} = \frac{Z_{0T}^2}{Z_L}$$

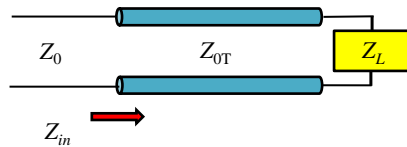

$$\Gamma_{in} = 0 \Rightarrow Z_{in} = Z_0$$

$$\Rightarrow Z_0 = \frac{Z_{0T}^2}{Z_L}$$

This requires  $Z_L$  to be real.

Hence

$$Z_{0T} = [Z_0 Z_L]^{1/2}$$

54


Consider the standing wave patterns as in Figure 11.23(a). From this, we observe that

$$\frac{\lambda}{2} = 19 - 11 = 8 \text{ cm} \quad \text{or} \quad \lambda = 16 \text{ cm}$$


$$f = \frac{u}{\lambda} = \frac{3 \times 10^8}{16 \times 10^{-2}} = 1.875 \text{ GHz}$$

Electrically speaking, the load can be located at 16 cm or 24 cm. If we assume that the load is at 24 cm, the load is at a distance  $\ell$  from  $V_{\min}$ , where

$$\ell = 24 - 19 = 5 \text{ cm} = \frac{5}{16} \lambda = 0.3125 \lambda$$

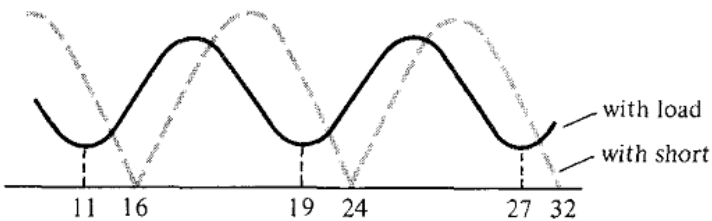

**Figure 11.23** Determining  $Z_L$  using the slotted line: (a) wave pattern, (b) Smith chart for Example 11.6.

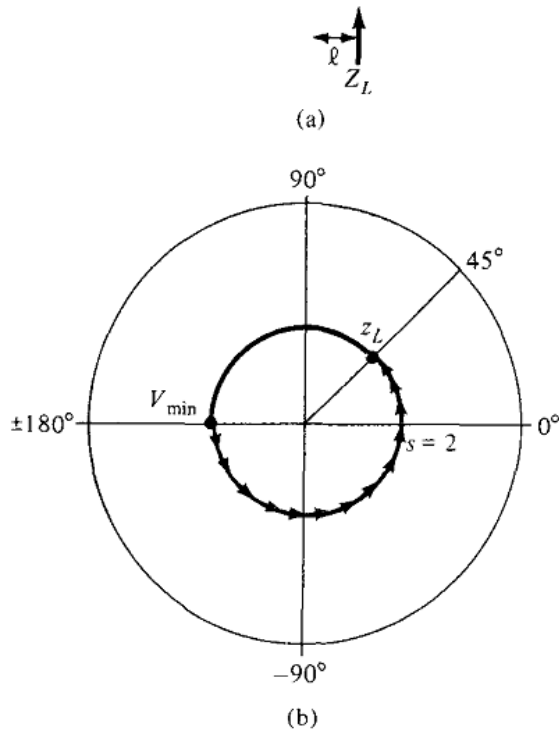

This corresponds to an angular movement of  $0.3125 \times 720^\circ = 225^\circ$  on the  $s = 2$  circle. By starting at the location of  $V_{\min}$  and moving  $225^\circ$  toward the load (counterclockwise), we reach the location of  $z_L$  as illustrated in Figure 11.23(b). Thus

$$z_L = 1.4 + j0.75$$

and

$$Z_L = Z_0 z_L = 50 (1.4 + j0.75) = 70 + j37.5 \Omega$$

#### Solution Question 5

Solution:

1. a) compute  $\Gamma_{in}$  and write it in terms of  $\Gamma_{short}$  for a lossy transmission-line

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = 0.915 e^{-j0.675} = \Gamma_{short} e^{-2\alpha\ell} e^{-j2\beta\ell}$$

knowing that  $\Gamma_{short} = -1 = e^{j\pi}$ , we can match magnitudes and phases

$$e^{-2\alpha\ell} = 0.915 \Rightarrow \alpha = \frac{1}{2(1.5)} \ln\left(\frac{1}{0.915}\right) = 0.0297 \text{ Np/m}$$

$$-2\beta\ell + \pi = -0.675 \Rightarrow \beta = \frac{0.675 + \pi}{2(1.5)} = 1.27 \text{ rad/m}$$

- b) compute  $\Gamma_L$  from which you can calculate  $\Gamma_{in}$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = -0.2 + j0.4$$

$$\Gamma_{in} = \Gamma_L e^{-2\alpha\ell} e^{-j2\beta\ell} = \frac{\Gamma_L}{\Gamma_{short}} \Gamma_{in}^{(a)} = (0.2 - j0.4)(0.915 e^{-j0.675}) = -0.0857 - j0.4$$

now convert this reflection coefficient to an impedance

$$Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 62.2 - j59.8 \Omega$$


- c) we apply the same equation as in part a) but with a new  $\ell$  and using  $\lambda = 2\pi/\beta = 4.94 \text{ m}$

$$\Gamma_{in} = \Gamma_{short} e^{-j2\beta\ell} e^{-2\alpha\ell} = -e^{-j2(2\pi)(0.15)} e^{-2(0.0297)(0.15)(4.94)} = 0.296 + j0.910$$

and convert to

$$Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 6.36 + j137 \Omega$$

6a)

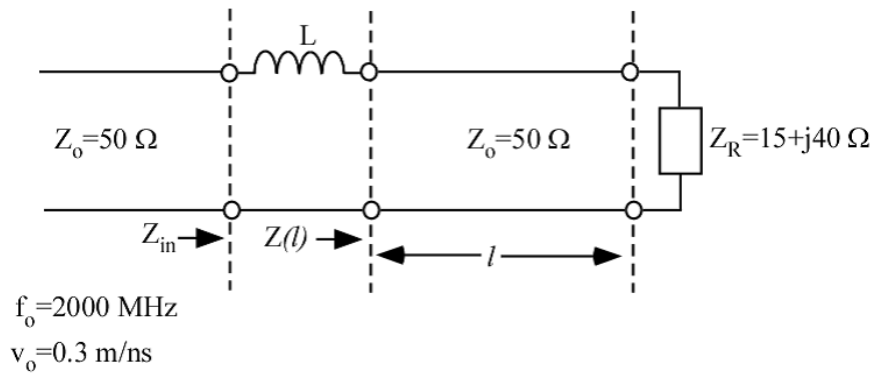

(a) Using the Smith chart, determine the SWR on the section of line of length  $l$ .

$$\lambda = \frac{v_0}{f_0} = \frac{0.3}{2 \times 10^9} = 15 \text{ cm}$$

$$15 + j40 \Omega \Rightarrow z_R = \frac{15 + j40}{50} = 0.3 + j0.8$$

From Smith chart, VSWR=5.7

$$\text{SWR} = 5.7$$

(b) Using the Smith chart find two values for the length  $l$  such that  $Z(l)$  is equal to  $Z_0 \pm jX$ .

$$l_1 = 0.186\lambda - 0.112\lambda = 0.074\lambda = 0.074 \times 15 = 1.11 \text{ cm}$$

$$l_2 = 0.313\lambda - 0.112\lambda = 0.201\lambda = 0.201 \times 15 = 3.015 \text{ cm}$$

$$Z(l_1) = Z_0 + jX, l_1 = 1.11 \text{ cm}$$

$$Z(l_2) = Z_0 - jX, l_2 = 3.015 \text{ cm}$$


(c) Determine the value of series inductance  $L$  and the proper length of the transmission line section ( $l_1$  or  $l_2$ ) that insures  $Z_{in} = Z_0$

Impedance is capacitive at  $l_2$  with  $z = 1 - j1.9$  or  $Z = 50 - j95 \Omega$ . Can be compensated with inductor such that

$$L = \frac{95}{2\pi \times 2 \times 10^9} = 7.55 \text{ nH} \quad L = 7.55 \text{ (nanoHenries)}$$




# IMPEDANCE OR ADMITTANCE COORDINATES

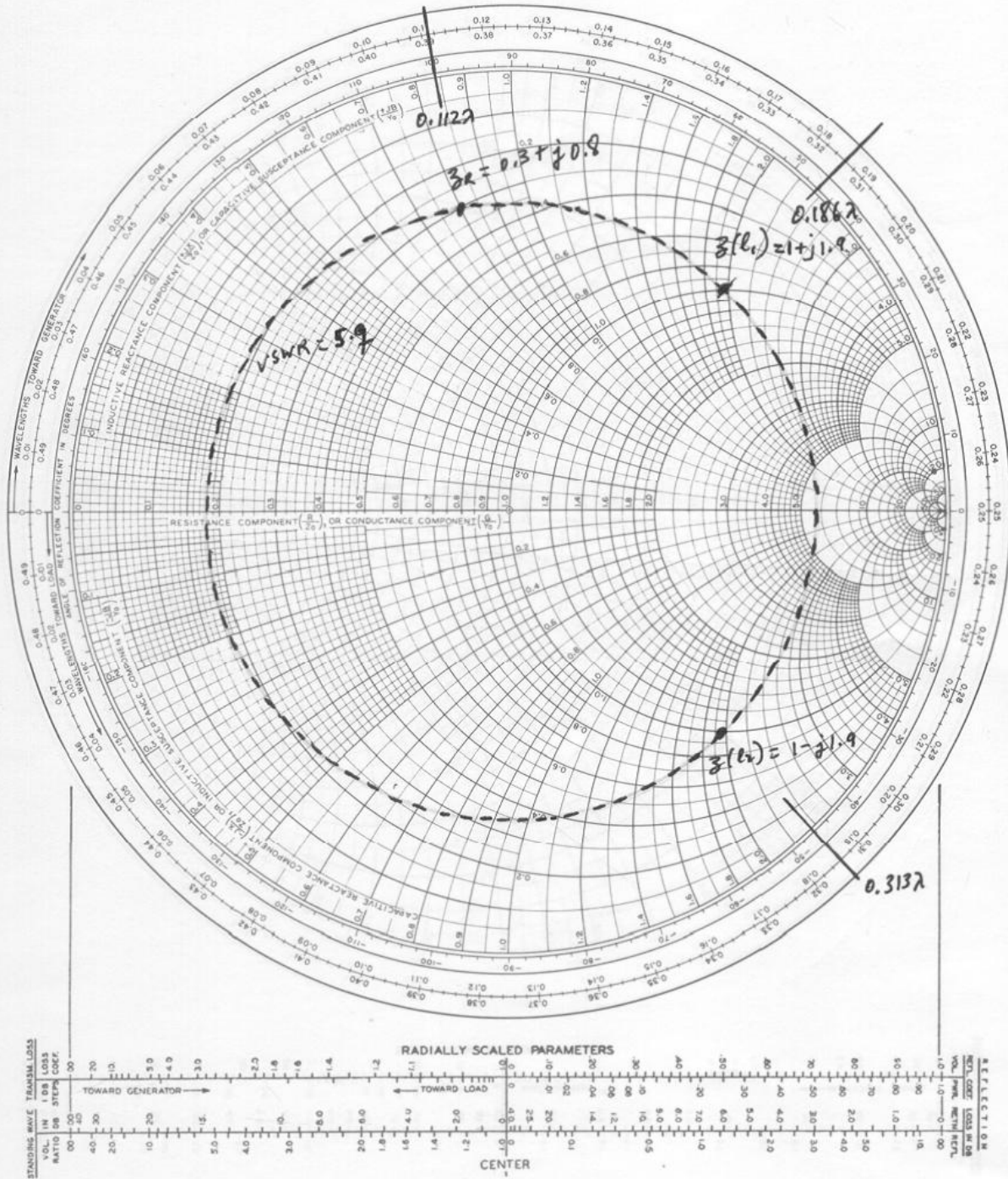

# Solution Question 6d

Solution:

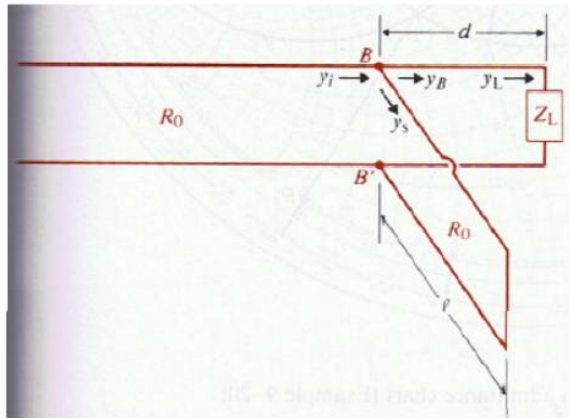

$$z_L = \frac{Z_L}{Z_0} = \frac{100 + j80}{75} = 1.33 + j1.07.$$

- Enter  $z_L$  (P1) on the Smith chart.
- Draw the SWR circle for the P1 (light blue).
- Transform into admittance  $y_L$  (P2).
- Travel towards generator until the intersection of the SWR circle and the  $g = 1$  circle.
- Intersections:
  - At P3:  $y_{B1} = 1 + j0.98 \Rightarrow y_{s1} = -j0.98$ ;  $d_1 = (0.161 - 0.432 + 0.5)\lambda = 0.229\lambda$
  - At P4:  $y_{B2} = 1 - j0.98 \Rightarrow y_{s2} = +j0.98$ ;  $d_2 = (0.339 - 0.432 + 0.5)\lambda = 0.407\lambda$

b) Using a short-circuited stub:

Match from P3:  $l_{1,SC} = (0.377 - 0.25)\lambda = 0.127\lambda$ ; (dark blue arrow)

Match from P4:  $l_{2,OC} = (0.123 - 0.25 + 0.5)\lambda = 0.373\lambda$ ; (dark blue dashed arrow)

