

**The LNM Institute of Information Technology, Jaipur**  
**Electronics and Communication Engineering Department**

**Engineering Electromagnetics(ECE335)**

**Exam Type:** Mid Term

**Academic Year:** 2017-18

**Semester:** ODD

**Degree:** B.Tech

**Programme:** ECE

**Year:** 2<sup>nd</sup> and 3<sup>rd</sup>

**Time :** 90 minutes

**Date:**28/09/2017

**Full Marks:** 50

	CO1	CO2	CO3	CO4	CO5
Questions	1,2,5a	3,4,5b,5c,6	-	-	-
Marks	20	30	-	-	-
Marks/Max Marks (%)	40	60	-	-	-

**Instruction:** No query will be entertained during examination. If you think any data is missing, assume suitable values. Write answer to all parts of question in same place. Write Roll no on top right corner of the smith chart. You can solve question by Smith Chart also.

[Q1]. (a) In the following circuit interconnection between Two Port Networks  $T_1$  and  $T_2$  is shown. Find ratio between  $V_1$  and  $V_2$ .

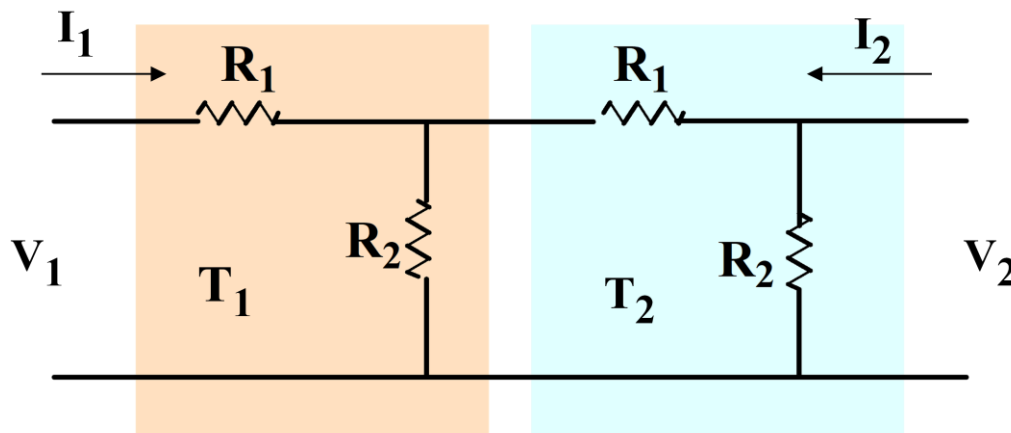


Figure 1. Cascaded Two Port Network

(b) Given  $Z_0$  equal to  $50 \Omega$ , find  $S_{11}$  and  $S_{22}$  for the circuit given in figure 2.

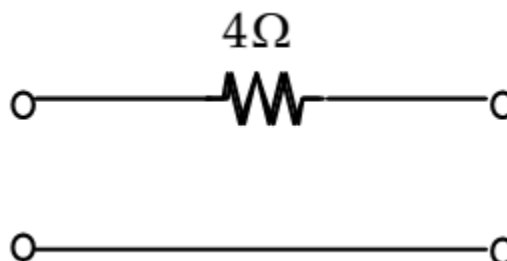



Figure 2. Circuit for question 1b

[3+3+2+2=10]

[Q2]. (a) A signal with power 3mW is distorted by noise with power -30dBm. What is the signal to noise Ratio( SNR) in dB.

(b) Prove that Noise Figure of a system as represented in following figure is given by,

$$F = \left( 1 + \frac{T_e}{T_{in}} \right) \Big|_{T_{in}=290K}$$

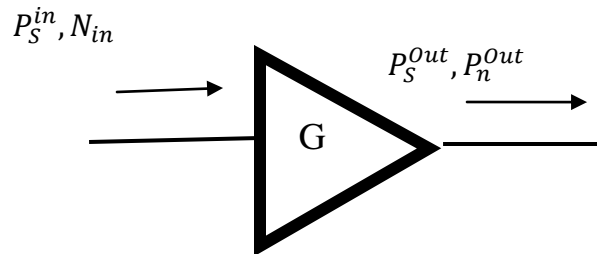

[2+3+3=8]

[Q3]. (a) In the circuit given in figure 3, calculate maximum power output from source with impedance  $Z_S$  that can be absorbed into load.

(b) The power flow into a one-port circuit can be written in the following form  $P_{in} = P_{AVS} - P_r$ , where  $P_{AVS}$  is the available power from the source. Assume source is sinusoidal and in steady state. If the source has a real resistance  $Z_0$  and it emitting complex power, then show that

$$P_r = P_{avs} \left| \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right|^2$$

(c) If  $P_{AVS} = P_{Load}$ , find  $S_{11}$  for the circuit in figure 3.


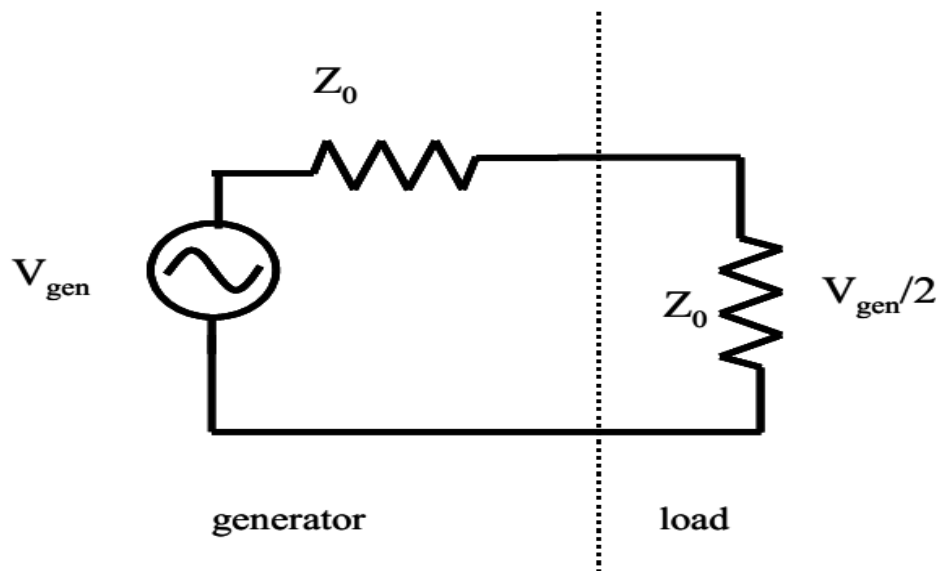


Figure 3. Circuit for Question 3.

[2+2+2=6]

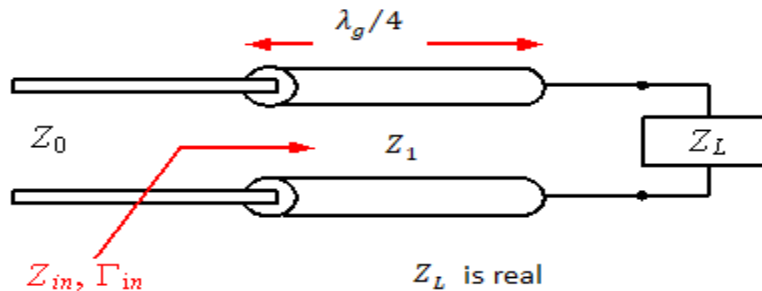- [Q4].** (a) Derive the input impedance formula for a lossless transmission line.  
(b) Find the input impedance for the transmission line given below.



- (c) A unknown load connected to a slotted air line, produces a SWR,  $S=2$  by the standing wave indicator and minimas are found at 14cm, 22cm, 30 cm..on the scale. when the load is replaced by a short circuit, the minimas are at 19cm, 27cm, 35cm .. If  $Z_0$  is  $50 \Omega$ , calculate the value of  $Z_L$ .

[4+3+3=10]


- [Q5].** The input impedance of a short-circuited lossy transmission line of length 1.5 m ( $< \lambda/2$ ) and a characteristic impedance of  $100 \Omega$  (approximately real) is  $40 - j280 \Omega$ .

- (a) Find  $\alpha$  and  $\beta$  of the line.  
(b) Determine the input impedance if the short-circuit is replaced by a load resistance  $Z_L = 50 + j50 \Omega$ .  
(c) Find the input impedance of the short-circuited line for a line length of  $0.15 \lambda$ .

[2+2+2=6]

- [Q6.]** Consider the lossless transmission line network shown below. The operating frequency is 2000 MHz and the propagation velocity on the transmission line is 0.3 m/ns.

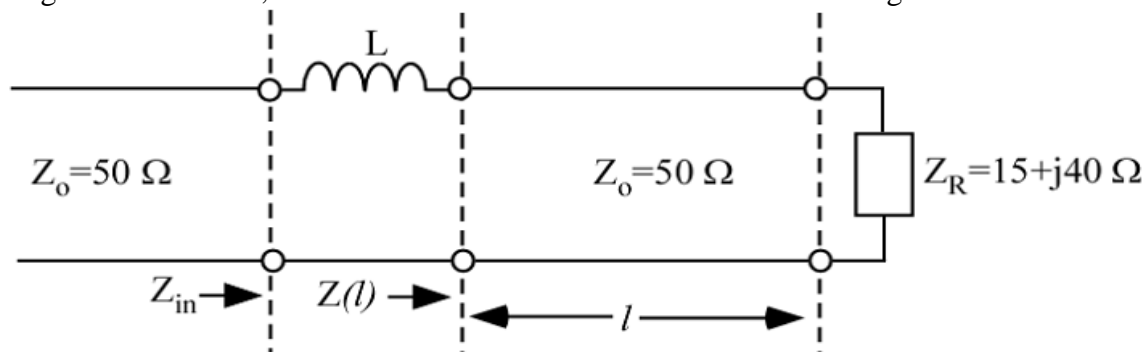- (a) Using the Smith chart, determine the SWR on the section of line of length  $l$



- (b) Using the Smith chart find two values for the length  $l$  such that  $Z(l)$  is equal to  $Z_0 \pm jX$ .  
(c) Determine the value of series inductance  $L$  and the proper length of the transmission line section ( $l_1$  or  $l_2$ ) that insures  $Z_{in} = Z_0$   
(d) Match a load impedance  $Z_L = (100 + j80) - \Omega$  to a line with characteristic impedance  $Z_0 = 75 - \Omega$  using a shunt single-stub tuner. Find solution using a short-circuited stub.

[2+2+2+4=10]


## Formula sheet

### Transmission line equations

$$\Gamma(-l) = \Gamma_R e^{-j2\beta l} = \frac{Z_R - Z_0}{Z_R + Z_0} e^{-j2\beta l}$$

$$Z(-l) = Z_0 \left[ \frac{Z_R + jZ_0 \tan \beta l}{Z_0 + jZ_R \tan \beta l} \right]$$
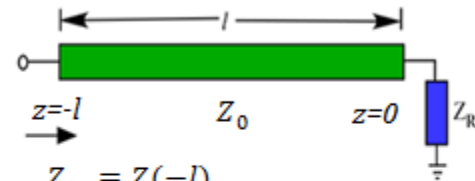
$$Z(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \quad \Gamma(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$



$$Z_{in} = Z(-l)$$

$$V(z) = V_+ e^{-j\beta z} [1 + \Gamma_R e^{+2j\beta z}]$$

$$I(z) = \frac{V_+}{Z_0} e^{-j\beta z} [1 - \Gamma_R e^{+2j\beta z}]$$

$$\beta = \frac{2\pi}{\lambda} = \frac{\omega}{v}$$

$$\Gamma_{in} = \Gamma_{short} e^{-j2\beta l} e^{-2\alpha l}$$

$$\Gamma_{in} = \Gamma_L e^{-2\alpha l} e^{-j2\beta l}$$

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

If there is a replacement of load then

$$\Gamma_{in}^2 = \frac{\Gamma_L}{\Gamma_{short}} \Gamma_{in}^1$$

S parameter :

$$S_{ij} \stackrel{\text{def}}{=} \left. \frac{b_i}{a_j} \right|_{a_i=0}$$